

تم تحميل هذا الملف من موقع المناهج الإماراتية



الملف اختبار في الكهربية الـ وحتين الخامسة والسادسة مع الحل

موقع المناهج ← المناهج الإماراتية ← الصف الثاني عشر المتقدم ← رياضيات ← الفصل الثاني

روابط مواقع التواصل الاجتماعي بحسب الصف الثاني عشر المتقدم



روابط مواد الصف الثاني عشر المتقدم على تلغرام

[الرياضيات](#)

[اللغة الانجليزية](#)

[اللغة العربية](#)

[التربية الاسلامية](#)

المزيد من الملفات بحسب الصف الثاني عشر المتقدم والمادة رياضيات في الفصل الثاني

[كل ما يخص الاختبار التكويني لمادة الرياضيات للصف الثاني عشر](#)  
[يوم الأحد 9/2/2020](#)

1

[تدريبات متنوعة مع الشرح على الوحدة الرابعة \(النهايات والاتصال\)](#)

2

[تدريبات متنوعة على تطبيقات الاشتقاق](#)

3

[قوانين هندسية](#)

4

[الاختبار القياسي في الرياضيات](#)

5

## اختبار في الكهرباء الوحدة 5 و 6 مع سلسلة أينشتاين الخليج

1. A light bulb is rated at 30 W when operated at 120 V. How much charge enters (and leaves) the light bulb in 1.0 min?
  - a. 17 C
  - b. 15 C**
  - c. 14 C
  - d. 13 C
  - e. 60 C
2. What maximum power can be generated from an 18-V *emf* using any combination of a 6.0  $\Omega$  resistor and a 9.0  $\Omega$  resistor?
  - a. 54 W
  - b. 71 W
  - c. 90 W**
  - d. 80 W
  - e. 22 W
3. If  $5.0 \times 10^{21}$  electrons pass through a 20  $\Omega$  resistor in 10 min, what is the potential difference across the resistor?
  - a. 21 V
  - b. 32 V
  - c. 27 V**
  - d. 37 V
  - e. 54 V
4. A wire (length = 2.0 m, diameter = 1.0 mm) has a resistance of 0.45  $\Omega$ . What is the resistivity (in  $\Omega \cdot \text{m}$ ) of the material used to make the wire?
  - a.  $5.6 \times 10^{-7}$
  - b.  $1.2 \times 10^{-7}$
  - c.  $1.8 \times 10^{-7}$**
  - d.  $2.3 \times 10^{-7}$
  - e.  $7.1 \times 10^{-7}$

5. Most telephone cables are made of copper wire of either 24 or 26 gauge. If the resistance of 24-gauge wire is  $137 \, \Omega$  /mile and the resistance of 26-gauge wire is  $220 \, \Omega$  /mile, what is the ratio of the diameter of 24-gauge wire to that of 26-gauge wire?
- 1.6
  - 1.3
  - 0.62
  - 0.79
  - 0.88
6. A conductor of radius  $r$ , length  $l$  and resistivity  $\rho$  has resistance  $R$ . What is the new resistance if it is stretched to 4 times its original length?
- $\frac{1}{16}R$
  - $\frac{1}{4}R$
  - $R$
  - $4R$
  - $16R$
7. A small bulb is rated at 7.5 W when operated at 125 V. Its resistance (in ohms) is
- 0.45.
  - 7.5.
  - 17.
  - 940.
  - 2100.
8. A small bulb is rated at 7.5 W when operated at 125 V. The tungsten filament has a temperature coefficient of resistivity  $\alpha = 4.5 \times 10^{-3} / ^\circ\text{C}$ . When the filament is hot and glowing, its temperature is seven times room temperature ( $20^\circ\text{C}$ ). What is the resistance of the filament (in ohms) at room temperature?
- 1280.
  - 1350.
  - 1911.
  - 455.
  - 630.


سلسلة أينشتاين الخليج  
Mr. Rami

9. The electron density in copper is  $8.49 \times 10^{28}$  electrons/m<sup>3</sup>. The electron charge is  $e = 1.6 \times 10^{-19}$  C. When a 1.00 A current is present in a copper wire with a 0.40 cm<sup>2</sup> cross-section, the electron drift velocity (in m/s), with direction defined relative to the current density, is

- a.  $-1.84 \times 10^{-6}$ .
- b.  $+1.84 \times 10^{-6}$ .
- c.  $-1.8$ .
- d.  $-5.43 \times 10^5$ .
- e.  $+5.43 \times 10^5$ .


10. What is the magnitude of the potential difference across the 20  $\Omega$  resistor?

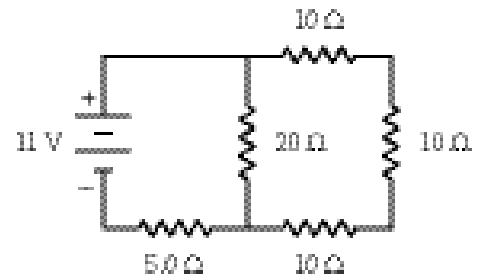- a. 3.2 V
- b. 7.8 V
- c. 11 V
- d. 5.0 V
- e. 8.6 V



11. At what rate is thermal energy generated in the 5  $\Omega$  resistor when  $\mathcal{E} = 24$  V?

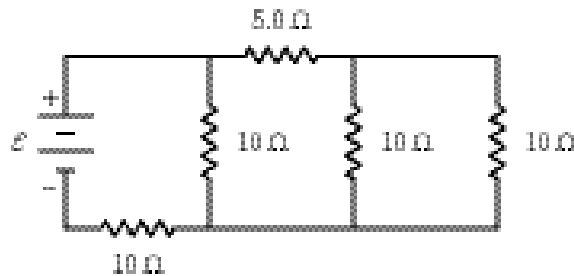- a. 13 W
- b. 3.2 W
- c. 23 W
- d. 39 W
- e. 51 W



12. When a 20-V *emf* is placed across two resistors in series, a current of 2.0 A is present in each of the resistors. When the same *emf* is placed across the same two resistors in parallel, the current through the *emf* is 10 A. What is the magnitude of the greater of the two resistances?

- a. 7.2  $\Omega$
- b. 7.6  $\Omega$
- c. 6.9  $\Omega$
- d. 8.0  $\Omega$
- e. 2.8  $\Omega$


13. A resistor of unknown resistance and a  $15\ \Omega$  resistor are connected across a  $20\text{-V}$  *emf* in such a way that a  $2.0\text{ A}$  current is observed in the *emf*. What is the value of the unknown resistance?

a.  $75\ \Omega$   
b.  $12\ \Omega$   
c.  $7.5\ \Omega$   
**d.  $30\ \Omega$**   
e.  $5.0\ \Omega$

Mr.Rami سلسلة أينشتاين الخليج


14. Determine  $\varepsilon$  when  $I = 0.50\text{ A}$  and  $R = 12\ \Omega$ .

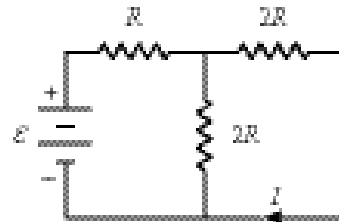a.  $12\text{ V}$   
**b.  $24\text{ V}$**   
c.  $30\text{ V}$   
d.  $15\text{ V}$   
e.  $6.0\text{ V}$




15. Determine the current in the  $10\text{-V}$  *emf*.

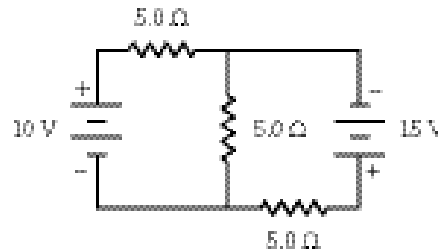**a.  $2.3\text{ A}$**   
b.  $2.7\text{ A}$   
c.  $1.3\text{ A}$   
d.  $0.30\text{ A}$   
e.  $2.5\text{ A}$




16. Determine the magnitude and sense (direction) of the current in the  $500\ \Omega$  resistor when  $I = 30\text{ mA}$ .

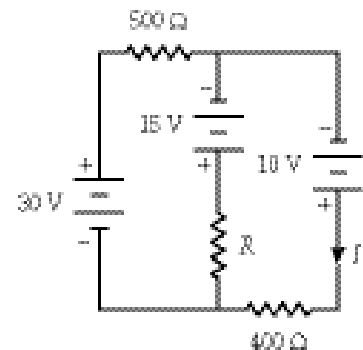**a.  $56\text{ mA}$  left to right**  
b.  $56\text{ mA}$  right to left  
c.  $48\text{ mA}$  left to right  
d.  $48\text{ mA}$  right to left  
e.  $26\text{ mA}$  left to right



17. What is the potential difference  $V_B - V_A$  when the  $I = 1.5\text{ A}$  in the circuit segment below?

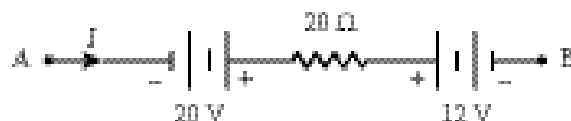
a.  $+22\text{ V}$   
**b.  $-22\text{ V}$**   
c.  $-38\text{ V}$   
d.  $+38\text{ V}$   
e.  $+2.0\text{ V}$



Mr.Rami سلسلة أينشتاين الخليج

18. If  $\varepsilon_1 = 4.0 \text{ V}$ ,  $\varepsilon_2 = 12.0 \text{ V}$ ,  $R_1 = 4 \Omega$ ,  $R_2 = 12 \Omega$ ,  $C = 3 \mu\text{F}$ ,  $Q = 18 \mu\text{C}$ , and  $I = 2.5 \text{ A}$ , what is the potential difference  $V_a - V_b$ ?

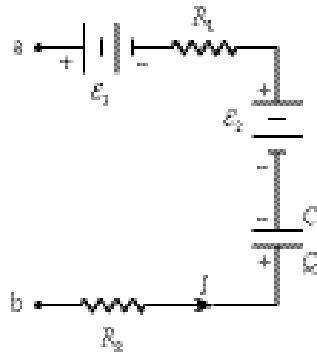
- a. -30 V
- b. 30 V
- c. 5.0 V
- d. -5.0 V
- e. -1.0 V



19. If  $I = 0.40 \text{ A}$  in the circuit segment shown below, what is the potential difference  $V_a - V_b$ ?

- a. 31 V
- b. 28 V
- c. 25 V
- d. 34 V
- e. 10 V

Mr.Rami سلسلة أينشتاين الخليج

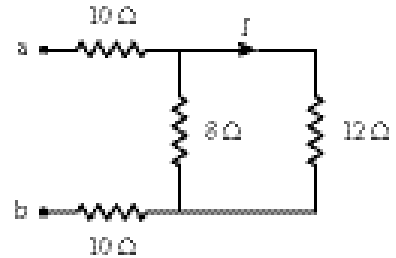

20. In an  $RC$  circuit, how many time constants must elapse if an initially uncharged capacitor is to reach 80% of its final potential difference?

- a. 2.2
- b. 1.9
- c. 1.6
- d. 3.0
- e. 5.0


Mr.Rami سلسلة أينشتاين الخليج

21. How many time constants must elapse if an initially charged capacitor is to discharge 55% of its stored energy through a resistor?

- a. 0.60
- b. 0.46
- c. 0.52
- d. 0.40
- e. 1.1

22. At  $t = 0$  the switch  $S$  is closed with the capacitor uncharged. If  $C = 30 \mu\text{F}$ ,  $\varepsilon = 30 \text{ V}$ , and  $R = 5.0 \text{ k}\Omega$ , at what rate is energy being stored in the capacitor when  $I = 2.0 \text{ mA}$ ?

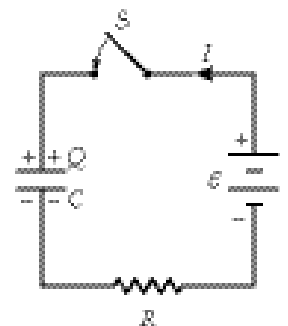
- a. 32 mW
- b. 40 mW
- c. 44 mW
- d. 36 mW
- e. 80 mW



Mr.Rami سلسلة أينشتاين الخليج


23. At  $t = 0$  the switch  $S$  is closed with the capacitor uncharged. If  $C = 40 \mu\text{F}$ ,  $\mathcal{E} = 50 \text{ V}$ , and  $R = 5.0 \text{ k}\Omega$ , how much energy is stored by the capacitor when  $I = 2.0 \text{ mA}$ ?

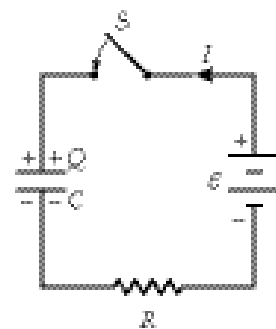a. 20 mJ  
b. 28 mJ  
c. 32 mJ  
d. 36 mJ  
e. 40 mJ




24. What is the equivalent resistance between points a and b when  $R = 30 \Omega$ ?

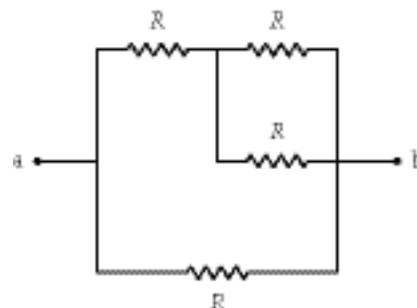a.  $27 \Omega$   
b.  $21 \Omega$   
c.  $24 \Omega$   
d.  $18 \Omega$   
e.  $7.5 \Omega$




25. What is the equivalent resistance between points a and b when  $R = 12 \Omega$ ?

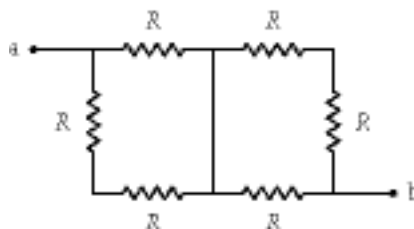a.  $20 \Omega$   
b.  $16 \Omega$   
c.  $24 \Omega$   
d.  $28 \Omega$   
e.  $6.0 \Omega$



26. What is the equivalent resistance between points A and B in the figure when  $R = 20 \Omega$ ?

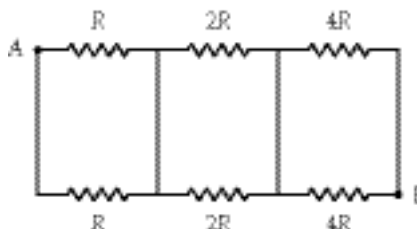a.  $77 \Omega$   
b.  $63 \Omega$   
c.  $70 \Omega$   
d.  $84 \Omega$   
e.  $140 \Omega$



27. In a loop in a closed circuit, the sum of the currents entering a junction equals the sum of the currents leaving a junction because

a. the potential of the nearest battery is the potential at the junction.  
b. there are no transformations of energy from one type to another in a circuit loop.  
c. capacitors tend to maintain current through them at a constant value.  
d. current is used up after it leaves a junction.  
e. charge is neither created nor destroyed at a junction.

28. The circuit below contains three 100W light bulbs. The  $emf \mathcal{E} = 110 \text{ V}$ . Which light bulb(s) is(are) brightest?


a. A

b. B

c. C

d. B and C

e. All three are equally bright.

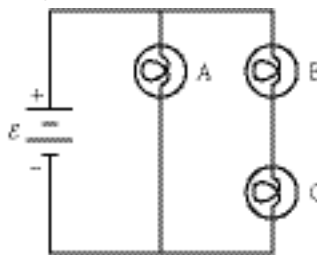

29. The circuit below contains three light bulbs and a capacitor. The  $emf \mathcal{E} = 110\text{V}$ . The capacitor is fully charged. Which light bulb(s) is (are) dimmest?


a. A

b. B

c. C

d. A and B

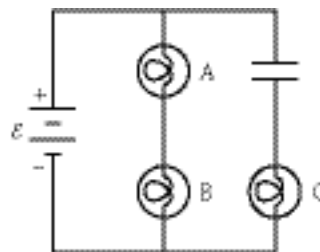e. All three are equally bright (or dim).



30. The circuit below contains three light bulbs and a capacitor. The  $emf$  is  $110 \text{ V}$  and the capacitor is fully charged. Which light bulb(s) is (are) brightest?


a. A

b. B

c. C

d. A and B

e. A and C

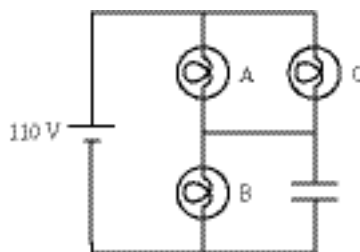

31. The capacitors are completely discharged in the circuit shown below.

The two resistors have the same resistance  $R$  and the two capacitors have the same capacitance  $C$ . After the switch is closed, the current

a. is greatest in  $C_1$ .

b. is greatest in  $C_2$ .

c. is greatest in  $R_1$ .

d. is greatest in  $R_2$ .

e. is the same in  $C_1$ ,  $C_2$ ,  $R_1$  and  $R_2$ .

