

شكراً لتحميلك هذا الملف من موقع المناهج الإماراتية



أسئلة المراجعة النهائية وفق الهيكل الوزاري

[موقع المناهج](#) ⇨ [المناهج الإماراتية](#) ⇨ [الصف الثاني عشر المتقدم](#) ⇨ [فيزياء](#) ⇨ [الفصل الثاني](#) ⇨ [الملف](#)

تاريخ نشر الملف على موقع المناهج: 12:12:50 2024-03-15

إعداد: [عبد الرحمن عصام](#)

التواصل الاجتماعي بحسب الصف الثاني عشر المتقدم



روابط مواد الصف الثاني عشر المتقدم على تلغرام

[الرياضيات](#)

[اللغة الانجليزية](#)

[اللغة العربية](#)

[التربية الاسلامية](#)

المزيد من الملفات بحسب الصف الثاني عشر المتقدم والمادة فيزياء في الفصل الثاني

[اختبار تجريبي الجزء الالكتروني وفق الهيكل](#)

1

[الحل التفصيلي للمراجعة النهائية للاختبار وفق الهيكل الوزاري](#)

2

[حل أسئلة وتدريبات وفق الهيكل الوزاري](#)

3


[أسئلة وتدريبات وفق الهيكل الوزاري](#)

4

[نموذج إجابة المراجعة النهائية للاختبار وفق الهيكل الوزاري](#)

5

ابن سينا

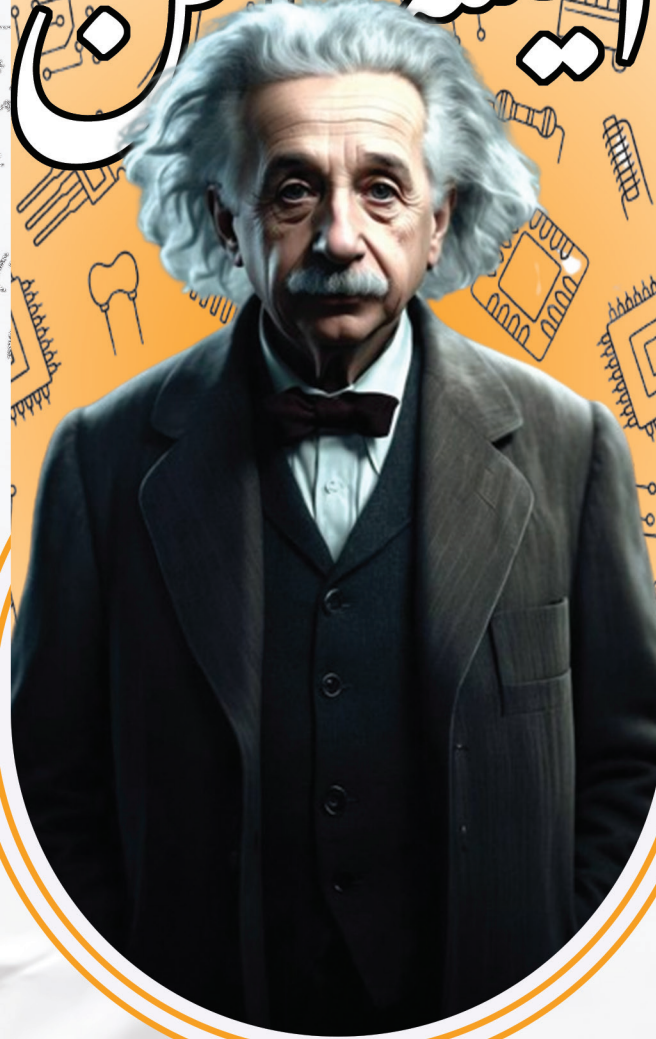

مراجعة الإلتقاذ في الفيزياء

مع خالص الدعاء بالتوفيق والنجاح

أ/ عبد الرحمن عصام

0509886279

Final Revision EoT2-Coverage-G12-Adv



Multiple Choice Questions Part

1 The total charge passing through a point in time is given by the formula.

(a) $q = \int_{t_i}^{t_f} i dt$

(c) $q = - \int_{t_i}^{t_f} i dt$

(b) $q = \int_{t_i}^{t_f} 2i dt^2$

(d) $q = \int_{t_i}^{t_f} \frac{1}{i} dt$

2 A metal wire in which an electric current flow and the amount of charge changes with time according to the equation ($q = 4t^2 - 3t + 1$) where q it is measured in unit coulomb .Calculate the magnitude of electric current flowing in the circuit at time ($t=2.0s$)

(a) 13A

(c) 26A

(b) 2A

(d) 16A

3 If the equation between charge and time is ($q=5t^2+3t$). What is the correct expression of the current (i)?

(a) $i = 10t + 3$

(c) $i = \frac{5t^3}{3} + \frac{3t}{2}$

(b) $i = 5t^2 + 3t$

(d) $i = 10t + 3t$

4 A metal wire carrying an electric current that changes in strength with time according to the equation $i = 6t^3 - 5t^2$ where I measured by unit ampere Calculate the amount of electric charge that passes through a section of wire during the time ($t=0.5s, t=2.0s$)

(a) 1.5C

(c) 10.8C

(b) 45.3C

(d) 37.8C

5 The number of charges that must flow through a device through (5s) for it to function normally is (6.4×10^{19}) What is the current flows through the device ?

(a) 3A

(c) 1A

(b) 2A

(d) 3A

6 A bolt of lightning has an electric current of $(3.5 \times 10^4 \text{ A})$ when hits the ground. If the lightning lasts for $(14 \mu\text{s})$, the amount of charges that is transferred to the ground is:

- (a) 0.50 C (c) $4.90 \times 10^2 \text{ C}$
(b) $4.9 \times 10^5 \text{ C}$ (d) 49.0 C

7 What is the current passing through a conductor with radius of (3.1 mm) , if the current density through this conductor is (5.2 A/m^2) ?

- (a) $1.6 \times 10^{-4} \text{ A}$ (c) $5.1 \times 10^{-2} \text{ A}$
(b) $3.5 \times 10^{-3} \text{ A}$ (d) $2.2 \times 10^{-4} \text{ A}$

8 Which of the following equations correctly represent the electric current in terms of the current density?

- (a) $i = \int \frac{1}{J} \cdot dA$ (c) $i = \int J^2 \cdot dA$
(b) $i = \int \frac{1}{J^2} \cdot dA$ (d) $i = \int J \cdot dA$

the wire ,it's a across section area A_1 . If the wire replaced with another its radius tribble the first wire . what will happen in current density through the second wire?

- (a) increase by factor 3 (c) increase by factor 9
(b) decrease by factor 1/9 (d) decrease by factor 1/3

9 A current of 0.123 mA flows in a silver wire whose cross-sectional area is 0.923 mm^2 . Find the current density in the wire assuming that the current is uniform.

- (a) 133.26 A/m^2 (c) 144.37 A/m^2
(b) 0.133 A/m^2 (d) 0.144 A/m^2

10 What is the current density in an aluminum wire having a radius of 1.00 mm and carrying a current of 1.00 mA?

- (a) 101.32 A/m^2 (c) 318.3 A/m^2
(b) 3.14 A/m^2 (d) 0.31 A/m^2

12 Which of the following is not true for current density(j) and current (i)?

- (a) Unit of current density equal to Ampere per Meter
- (b) Unit of current density equal to Ampere per Meter square
- (c) $j = \frac{i}{A}$
- (d) $i = \int j \cdot dA$

13 Two wires carry the same current, but if the area of the second wire is 3 times the area of the first wire, which of the following is true?

- (a) $J_2 = \frac{1}{9}J_1$
- (b) $J_2 = \frac{1}{3}J_1$
- (c) $J_2 = 9J_1$
- (d) $J_2 = 3J_1$

14 A potential difference of (18.0V) is used on a wire whose cross-sectional area(5.0mm²) and length is equal(370km) . The electric current flowing through the wire is (1.5×10⁻²A).

What is the material of the wire?

- (a) Iron
9.74×10⁻⁸ Ωm
- (b) Nichrome
108×10⁻⁸ Ωm
- (c) Copper
1.72×10⁻⁸ Ωm
- (d) Silver
1.62×10⁻⁸ Ωm

15 How will the resistance of a copper wire change if its length is tripled (without changing in its cross-sectional area)?

- (a) increase by factor 3
- (b) decrease by factor 1/9
- (c) increase by factor 9
- (d) decrease by factor 1/3

16 How will the resistance and current that flowing through a copper wire change if the radius of the wire is doubled?

- (a) increase by factor 4
- (b) decrease by factor 1/4
- (c) increase by factor 2
- (d) decrease by factor ½

What is the resistance (R) of a silver wire ($\rho=1.62 \times 10^{-8} \Omega \cdot m$), has a length of(3.0 m) and a radius of(52mm)?

- (a) $5.7 \times 10^{-6} \Omega$
- (b) $3.4 \times 10^{-6} \Omega$
- (c) $2.6 \times 10^{-6} \Omega$
- (d) $1.9 \times 10^{-6} \Omega$

18 The (2.0 m) length hollow silver tube shown in the figure has inner radius of (2.0 cm) and outer radius of (3.0 cm) what is the resistance of this conductor? ($\rho=1.62\times 10^{-8} \Omega.m$)

- (a) $1.0\times 10^{-5} \Omega$ (c) $3.6\times 10^{-5} \Omega$
(b) $2.1\times 10^{-5} \Omega$ (d) $4.4\times 10^{-5} \Omega$



19 Which of the following is equal to the unit of **siemens (S)**?

- (a) $1S = \frac{1A}{1V}$ (c) $1S = \frac{1A^2}{1V}$
(b) $1S = \frac{1V}{1A}$ (d) $1S = \frac{1V^2}{1A}$

A cylindrical aluminum wire is (32m) long and has a resistance 0.20Ω the resistivity of aluminum is ($2.82 \times 10^{-8} \Omega.m$). What is the radius?

- (a) $4.512 \times 10^{-6}m$ (c) $1.436 \times 10^{-6}m$
(b) $1.198 \times 10^{-3}m$ (d) $1.436 \times 10^{-3}m$

If the Conductance of the wire is $0.9S$, and there is another wire of the same material and the same length, and the radius of the second wire is 3 times that of the first wire, what is the Conductance of the second wire?


- (a) 0.9S (c) 2.7S
(b) 8.1S (d) 0.3S

What happens when the potential difference in a cylindrical conductor increases?

- (a) The current through the conducting cylinder decreases . (c) The current through the conducting cylinder increases .
(b) The resistance of the conducting cylinder increases . (d) The resistance of the conducting cylinder decreases.

For the electric circuit shown in the figure: if the battery's electromotive force is (12V), the resistance is ($R=2.4\Omega$), what is the electric current flowing through the circuit?


- (a) 5.0A (c) 28.8A
(b) 0.2A (d) 2.0A

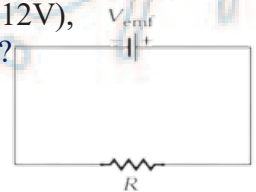

23

23 For the electric circuit shown in the figure: if the battery's electromotive force is (12V), the resistance is ($R=2.4\Omega$), what is the electric current flowing through the circuit?

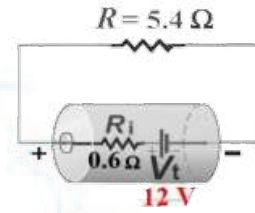- (a) 5.0 A (c) 0.2 A
(b) 28.8 A (d) 2.0 A




24 A 6.0 V battery with an internal resistance of 0.30Ω is connected to a 1.20Ω resistor. What is the electric current flowing through the circuit?

- (a) 5A (c) 9A
(b) 4A (d) 20A


25 Consider a battery that has ($V_t = 12.0\text{ V}$) when it is not connected to a circuit, When a (10.0Ω) resistor is connected with the battery, the potential difference across the battery's terminals drops to (10.9 V). What is the internal resistance of the battery?

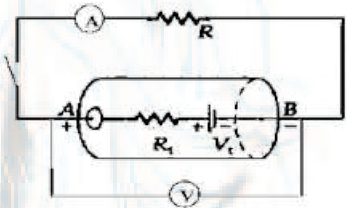- (a) 1.0Ω (c) 120.0Ω
(b) 2.3Ω (d) 109.0Ω



In the previous figure if the reading voltmeter when the circuit is open (12v) and when the circle was closed a voltmeter reading became (11.5v) and reading of ammeter (2A)
What is the internal resistance of the battery?

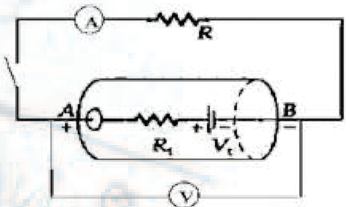- (a) 6.0Ω (c) 5.75Ω
(b) 0.25Ω (d) 11.75Ω



The quantity 1mAh is equal to

- (a) 3.6As (c) 3.6A
(b) 3.6C (d) A+B is correct

A rechargeable battery is rated at (3.0mAh). What is the total charge in Coulombs unit (C) of the battery can deliver when fully charged? (mAh means milliampere-hour)

- (a) 10.8C (c) 3.0C
(b) 3.6C (d) 1.6C


28

29 Which of the following is equivalent to 3.6 C ?

- (a) 1.0 milliampere. Hour (c) 1.0 ampere. Hour
(b) 1.0 ampere. Second (d) 1.0 milliampere. Second


The adjacent graph shows the voltage changes between the two terminals of a resistor and the current passing through it. What is the resistance?

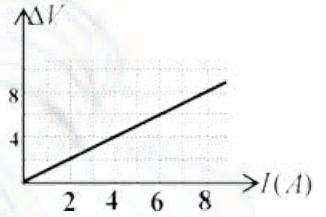- (a) 1.0 Ω (c) 0.5 Ω
(b) 2.3 Ω (d) 4.0 Ω




For the circuit shown in the figure, $R_1 = 2.0\ \Omega$, $R_2 = 1.0\ \Omega$, $R_3 = 5.0\ \Omega$, and the potential difference is 40 V . What is the current flowing through the circuit?

- (a) 8 A (c) 5 A
(b) 20 A (d) 40 A

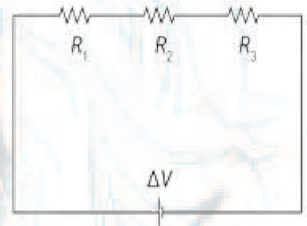


For the circuit shown in the figure, $R_1 = 3R_2$ and V_{emf} is 8.0 V . if a current of 0.2 A flows through the circuit What is the resistance of R_1 ?

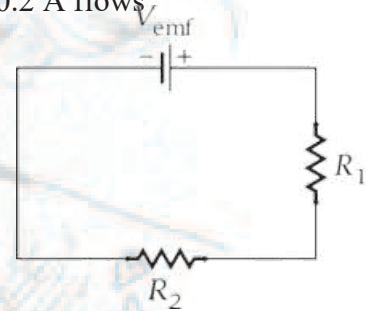- (a) 40.0 Ω (c) 20.0 Ω
(b) 10.0 Ω (d) 30.0 Ω




For the electric circuit shown in the figure, find the value of (R)

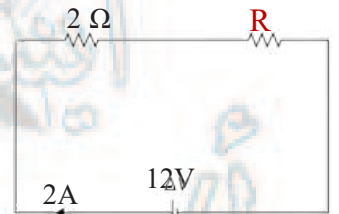- (a) 4.0 Ω (c) 6.0 Ω
(b) 8.0 Ω (d) 5.0 Ω




Based on the figure below which statement is true ?

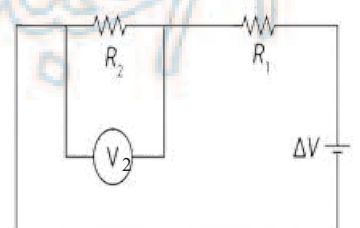- (a) $V_2 < V$ (c) $V_2 = V$
(b) $V_2 > V$ (d) $V_2 = 0$



35 According to the figure, when a third resistor is added in series to the two resistors connected in series . What happens to the electric current passing through the circuit?

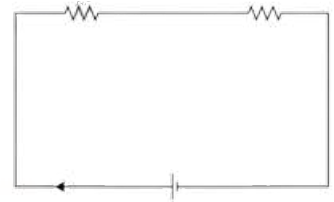- (a) Decrease (c) Stays the same
(b) Increase (d) Becomes infinity



36 Four resistors, 1.0Ω , 3.0Ω , 5.0Ω , and 4.0Ω , are connected in series with a 9.0 V battery. What is the equivalent resistance of the circuit?

- (a) 13.0Ω (c) 1.8Ω
(b) 6.0Ω (d) 0.6Ω

37 Abdelrahman connected eight 12Ω lamps in series . What is the total resistance of the circuit ?


- (a) 0.67Ω (c) 1.5Ω
(b) 12Ω (d) 96Ω

Which of the following is an incorrect statement?

- (a) More current flows across the smaller resistance when two resistors are connected in series. (c) More current flows across the smaller resistance when two resistors are connected in parallel.
(b) The potential drops across devices connected in parallel are equal. (d) The currents through devices connected in series are equal.


39 The electric potential difference between the battery terminals shown in the circuit is equal to ?

- (a) 12V (c) 6V
(b) 18V (d) 27V

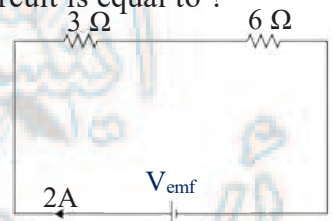

In the figure if the Voltmeter Reading is 24 V . then Amount of R_2 :

- (a) 12.0Ω (c) 4.0Ω
(b) 6.0Ω (d) 3.0Ω

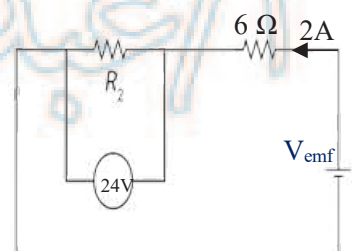


40

41 An electrical circuit consisting of three resistors connected in parallel, with a battery and a switch. The most important characteristic of this type of connection is that:

- (a) The total potential difference equals the sum of the potential difference between each
- (b) All of these resistors must have the same electrical current
- (c) When current stops flowing through one of these resistors, it stops flowing to the restrictors
- (d) The total current must be equal to the sum of the sub currents passing through these resistors


42 For the circuit shown in the figure, if another resistor with equal resistance was connected with R in parallel, what happens to the magnitude of the current flowing through the battery?

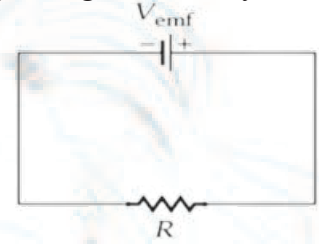- (a) Becomes twice
- (b) Stays the same
- (c) Becomes half
- (d) Becomes four times




43 What is the equivalent resistance of the circuit shown below ?

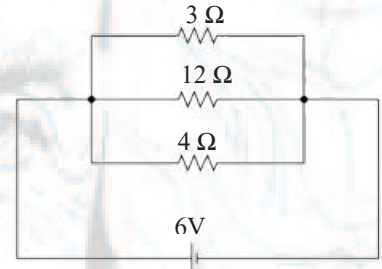- (a) 1.0Ω
- (b) 1.5Ω
- (c) $\frac{1}{19} \Omega$
- (d) 19.0Ω



44 What is the Current of the circuit shown below ?

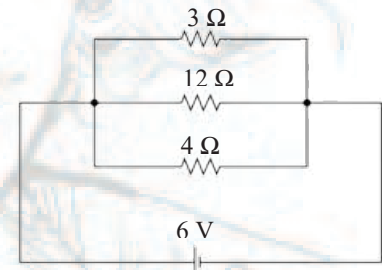- (a) 4A
- (b) 0.25 A
- (c) 0.32A
- (d) 3.2A




45 Three identical resistors connected together in parallel. If the equivalent of the three resistors is (6.0Ω) . What is the resistance of any resistor of them?

- (a) 4Ω
- (b) 2Ω
- (c) 6Ω
- (d) 18Ω

46 The amount of resistance R in the figure is equal :

- (a) 20Ω
- (b) 2Ω
- (c) 12Ω
- (d) 10Ω

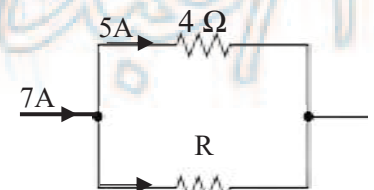

47 A parallel circuit has four branch currents: 120 mA ,250 mA ,380 mA ,and 1.25A.
How much current passes through the power source?

- (a) 0.75A (c) 2A
(b) 0.75mA (d) 2mA

48 Three equal resistors connected in parallel to a battery (12.0V) If a current of (1.5A).
What is the resistance of each of them?

- (a) 24Ω (c) 2.66 Ω
(b) 8 Ω (d) 1.5 Ω

49 An electrical device with a power of (968W) is connected to a source of
electromotive force (V =220V). What is the resistance of this device?

- (a) 50 Ω (c) 4.4 Ω
(b) 2 Ω (d) 0.23 Ω

A DC winch motor is rated at 20 A with a voltage of 115 V. What is the power consumed by
the motor?

- (a) 3300W (c) 2300W
(b) 200W (d) 1300W

A current of 6.0 A passes through a 325 W heater. What is the resistance of the heater?

- (a) 88 Ω (c) 54Ω
(b) 4.5 Ω (d) 9 Ω

An 80.0 W power filament bulb whose resistance is 45 Ω. what is the current passing
through the filament bulb?

- (a) 1.3A (c) 12A
(b) 0.56A (d) 1.8A

53 What is the potential difference between the two ends of the lamp whose resistance is 484Ω when operating at the power of $1.00 \times 10^2 \text{ W}$?


- (a) 220 V (c) 136 V
(b) 116 V (d) 48400 V

54 A 100W light bulb connected to a 120 V power line. The current in the light bulb is equal ?

- (a) 0.83A (c) 1.2A
(b) 0.38A (d) 2.1A


55 Four wires are connected to each other as shown to the right. The electric current passing through the red wire is

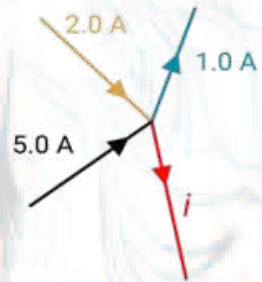- (a) 6.0 A (c) 3.0 A
(b) 8.0 A (d) 2.0 A




56 Four wires that carry different amounts of currents are connected to a single point as shown. The electric current through the blue wire is and the junction.

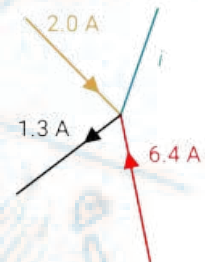- (a) 5.7A leaves (c) 7.1A leaves
(b) 9.7A enters (d) 7.1A enters




57 Which of the below choices are correct about the image shown?

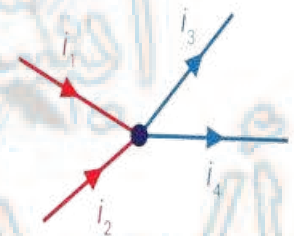- (a) $i_1 + i_2 = i_3 + i_4$ (c) $i_1 + i_4 = i_2 - i_3$
(b) $i_1 + i_3 = i_2 + i_4$ (d) $i_1 + i_4 = i_2 + i_3$




58 According to the figure, what is the magnitude and direction of (i)

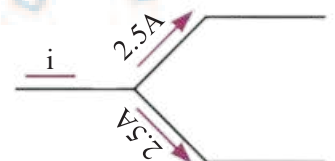- (a) 6.0A left (c) 1.0A right
(b) 1.0A left (d) 6.0A right




59 What is the current flowing through the loop shown in the figure?

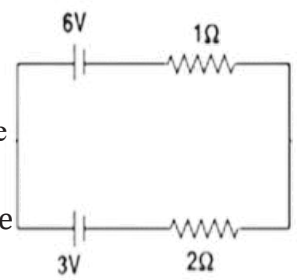- (a) 1A Clockwise (c) 1A Counterclockwise
(b) 2A Clockwise (d) 2A Counterclockwise



60 Two resistors are connected to two batteries as shown . What is the electric current flowing through the wires?

- (a) 6.0A (c) 0.33A
(b) -4.3A (d) 4.3A

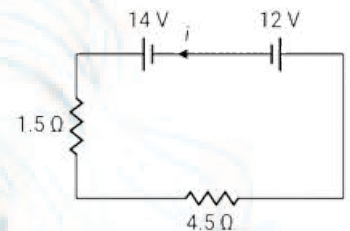

61 When analyzing loops in electric circuits, which of the following assumptions is correct for the conventions used to determine the sign of potential changes?

- (a)

| Element | Direction of Analysis | Potential Change |
|-----------|-----------------------|------------------|
| R | Same as current | $-iR$ |
| R | Opposite to current | $+iR$ |
| V_{emf} | Same as emf | $+V_{emf}$ |
| V_{emf} | Opposite to emf | $-V_{emf}$ |
- (b)


| Element | Direction of Analysis | Potential Change |
|-----------|-----------------------|------------------|
| R | Same as current | $+iR$ |
| R | Opposite to current | $-iR$ |
| V_{emf} | Same as emf | $+V_{emf}$ |
| V_{emf} | Opposite to emf | $-V_{emf}$ |
- (c)

| Element | Direction of Analysis | Potential Change |
|-----------|-----------------------|------------------|
| R | Same as current | $-iR$ |
| R | Opposite to current | $+iR$ |
| V_{emf} | Same as emf | $-V_{emf}$ |
| V_{emf} | Opposite to emf | $+V_{emf}$ |
- (d)

| Element | Direction of Analysis | Potential Change |
|-----------|-----------------------|------------------|
| R | Same as current | $+iR$ |
| R | Opposite to current | $-iR$ |
| V_{emf} | Same as emf | $-V_{emf}$ |
| V_{emf} | Opposite to emf | $+V_{emf}$ |


62 If the reading of the sensitive ammeter (A) is zero, what is the magnitude of R?

- (a) 8 Ω (c) 24 Ω
(b) 12 Ω (d) 4 Ω

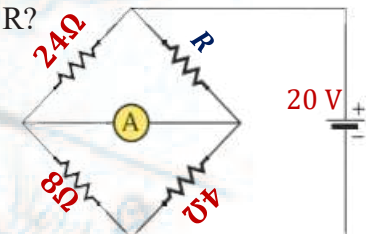


63 According to the figure, if the reading of the sensitive ammeter (A) is zero, ($R_1 = 6\Omega$), ($R_2 = 4\Omega$) and ($R_3 = 8\Omega$), what is the magnitude of (R_4)

- (a) 6 Ω (c) 18 Ω
(b) 12 Ω (d) 4 Ω

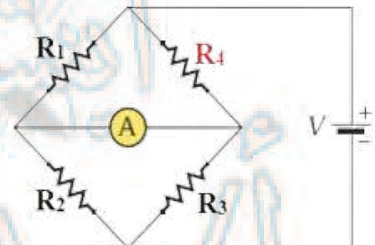


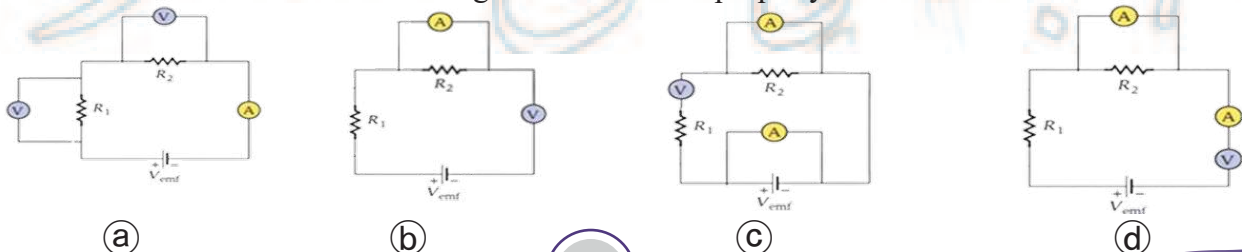64 Which of the circuits shown in the figure will function properly ?



65 Three voltmeters are shown in the figure. Which one will measure zero?

- (a) X (c) Z
(b) Y (d) Z, X

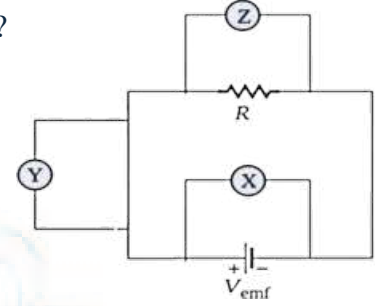

66 A resistor of resistance 1.5Ω is connected in series across a battery of electromotive force 9.0 V and a parallel-plate capacitor of capacitance $25\ \mu\text{F}$. What is the amount of charge on the plates of the capacitor after a time interval equal to the time constant?

- (a) $5.27 \times 10^{-4}\text{ C}$ (c) $1.42 \times 10^{-6}\text{ C}$
(b) $5.27 \times 10^{-6}\text{ C}$ (d) $1.42 \times 10^{-4}\text{ C}$

67 the RC circuit which $R = 1.50\text{ M}\Omega$, $C = 4.00\ \mu\text{F}$, and $V_{\text{emf}} = 25.0\text{ V}$. Find the time constant of the circuit.

- (a) 6 s (c) 4 s
(b) 0.75 s (d) 0.23 s

68 A series RC circuit for which $R = 1.0\text{ M}\Omega$, $C = 5.0\ \mu\text{F}$, and $V_{\text{emf}} = 30\text{ V}$. Find the charge on the capacitor 10 s after the switch is closed.

- (a) $1.30 \times 10^{-4}\text{ C}$ (c) $1.30 \times 10^{-6}\text{ C}$
(b) 5 C (d) $1.42 \times 10^{-4}\text{ C}$

69 If the time constant is 0.1 s and the resistance is $1000\ \Omega$, calculate the capacitance of the capacitor.


- (a) $1.0 \times 10^{-4}\text{ F}$ (c) $1.0 \times 10^3\text{ F}$
(b) $1.0 \times 10^{-1}\text{ F}$ (d) $6.0 \times 10^{-4}\text{ F}$

70 An RC circuit consisting of a (12.0 V) battery. The charge (q) the capacitor as a function of time is given by: $q(t) = 6.0 \times 10^{-4} (1 - e^{-\frac{t}{0.1}})$

- (a) $6.0 \times 10^{-4}\text{ F}$ (c) $6.0 \times 10^{-5}\text{ F}$
(b) $5.0 \times 10^{-5}\text{ F}$ (d) $7.2 \times 10^{-5}\text{ F}$


71 The figure shows the magnetic field lines of a permanent magnet. Which of the following is correct when determining the north pole and south pole of the magnet?

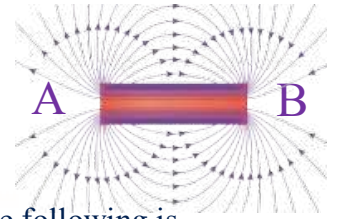- (a) B is the north pole (c) B is the south pole
(b) A is the north pole (d) There isn't enough data to determine the poles




The figure shows the magnetic field lines of a permanent magnet. Which of the following is correct when determining the north pole and south pole of the magnet?

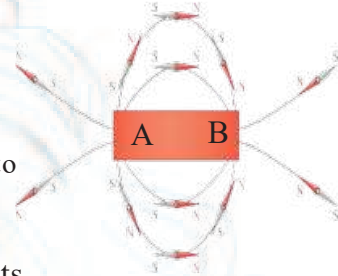- (a) B is the north pole (c) B is the south pole
(b) A is the north pole (d) There isn't enough data to determine the poles




The diagram below represents the magnetic field lines around two bar Magnets . Identify the poles at positions A and B.

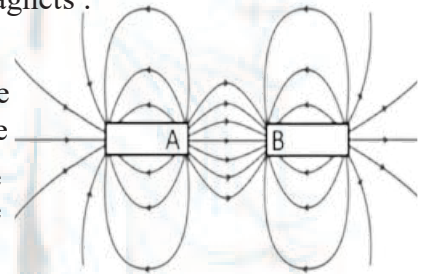- (a) A=north pole B=south pole (c) A=south pole B=south pole
(b) A=south pole B=north pole (d) A=north pole B=north pole




According to the figure, in what direction the proton (p) will be deflected as it enters the constant magnetic field (B) ?

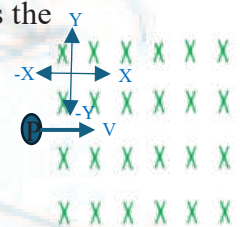- (a) Toward y positive (c) Into the page
(b) Toward y negative (d) Out of the page




According to the figure, in what direction the proton (p) will be deflected as it enters the constant magnetic field (B) ?

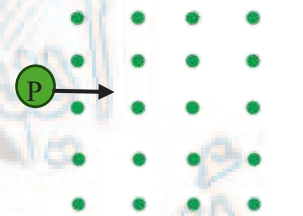- (a) Toward y positive (c) Into the page
(b) Toward y negative (d) Out of the page



A charged particle enters a uniform magnetic field as shown in the figure, what is the direction of the magnetic force that will exert on the particle?

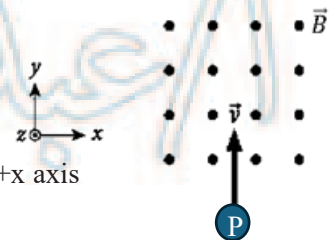- (a) To the direction of +y axis (c) To the direction of +x axis
(b) To the direction of -y axis (d) To the direction of -x axis



78 Which of the following is an equivalent unit of Tesla?

- (a) $\frac{N \cdot s}{C \cdot m}$ (c) $\frac{N}{A \cdot m}$
 (b) $\frac{N \cdot C}{s \cdot m}$ (d) A + C are correct

79 A charged particle with charge of $(3.2 \times 10^{-12} \text{ C})$, enters a uniform magnetic field, the charged particle follows a helical path with radius of (2.5 m) , if the perpendicular component of the charged particle momentum is $(1.6 \times 10^{-12} \text{ kg} \cdot \text{m/s})$, what is the magnitude of the magnetic field?

- (a) 0.20 T (c) 0.40 T
 (b) 0.30 T (d) 0.07 T

80 A particle with charge $(q = +3.2 \mu\text{C})$ and speed $(v = 520 \text{ m/s})$, enters a uniform magnetic field of $(B = 0.2 \text{ T})$ as seen in the figure. What is the magnitude of the magnetic force on the particle?

- (a) $332.8 \mu\text{N}$ (c) $3.2 \mu\text{N}$
 (b) $166.4 \mu\text{N}$ (d) $520 \mu\text{N}$

81 Proton moving with a speed of $4.00 \times 10^5 \text{ m/s}$ in the positive y-direction enters a uniform magnetic field of 0.400 T pointing in the positive z-direction. Calculate the magnitude of the force on the proton.

- (a) $2.56 \times 10^{-14} \text{ N}$ (c) $3.23 \times 10^{-12} \text{ N}$
 (b) $2.56 \times 10^{-19} \text{ N}$ (d) $3.23 \times 10^{-14} \text{ N}$

82 The magnitude of the magnetic force on a particle with charge $-2e$ moving with speed $v = 1.0 \times 10^5 \text{ m/s}$ is $3.0 \times 10^{-18} \text{ N}$. What is the magnitude of the magnetic field? $(e = 1.6 \times 10^{-19} \text{ C})$

- (a) $1.5 \times 10^{-23} \text{ T}$ (c) $1.5 \times 10^{-23} \text{ T}$
 (b) $1.9 \times 10^{-4} \text{ T}$ (d) $3.0 \times 10^{-23} \text{ T}$

83 In the equation $(B = \frac{mv}{|q|x})$, what does (x) represent ?

- (a) The radius (c) The angle
 (b) The diameter (d) The acceleration

84

According to the figure, an isolated segment of wire of length ($L=8.3\text{m}$) carries a current of magnitude ($i=1.5\text{A}$) at an angle ($\theta=60.0^\circ$) with respect to a constant magnetic field of magnitude ($B=5.4\times 10^{-2}\text{ T}$). What is the magnitude of the magnetic force on the wire?

- (a) 0.58N (c) 0.33N
(b) 0.29N (d) 2.16N

85

A straight wire of length (2.0m) and a current of (24.0A) is flowing in it on a horizontal table surface in a regular horizontal magnetic field, and the wire makes an angle ($\theta = 30^\circ$) with the magnetic field lines. If the magnitude of the magnetic force acting on the wire is (0.50N) What is the magnitude of the magnetic field?

- (a) 19.2T (c) 210 T
(b) 12 T (d) 0.21 T

86

A coil (X) consists of (400) loop and a coil (Y) consists (900) loop, If the torque on each loop of the coil (X) is equal to the torque on each loop of the coil (Y). What is the ratio of the torques (τ_X/τ_Y)

- (a) 2/3 (c) 4/9
(b) 3/2 (d) 9/4

Recall that the SI unit of magnetic field strength is Tesla (T)

87

$$[F_B] = [q][v][B] \Rightarrow [B] = \frac{[F_B]}{[q][v]} = \frac{\text{N s}}{\text{C m}} \quad 1 \text{ T} = 1 \frac{\text{N s}}{\text{C m}} = 1 \frac{\text{N}}{\text{A m}}$$

Apply the relationship between the magnetic force, charge q , velocity, and the magnetic field B . Apply Newton's second law, for a charged particle in uniform circular motion due to a magnetic force, to derive an expression for the orbital radius.

88

$$qvB = ma_{\text{c}} r = \frac{mv^2}{r} \quad B = \frac{mv}{qr} \quad B = \frac{F}{qv}$$

An electron enters a uniform magnetic field at a velocity of $2.0 \times 10^6 \text{ m/s}$ at right angle as shown in the figure. The field exerts a force of $5 \times 10^{-15} \text{ N}$ on the electron.

a- What is the **magnetic field** strength?

The charge of the electron is ($q_e = -1.6 \times 10^{-19} \text{ C}$)


2- What is the **direction** of the force acting on the electron?



89


.....

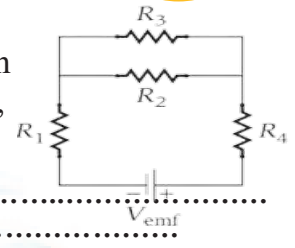90 The circuit shown in Figure has four resistors and a battery with $V_{emf} = 149 \text{ V}$. The values of the four resistors are $R_1 = 17.0 \Omega$, $R_2 = 51.0 \Omega$, $R_3 = 114.0 \Omega$, and $R_4 = 55.0 \Omega$. What is the magnitude of the **potential drop** across R_2 ?




.....
.....
.....

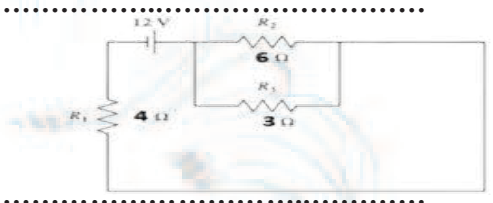91 According to the circuit bellow:
2) Find the current in R_3 .
3) Find the potential difference across R_2 .




.....
.....
.....
.....

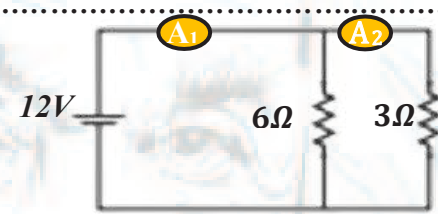92 According to the circuit bellow:
1) Find reading the ammeter A_1 .
2) Find reading the ammeter A_2




.....
.....
.....
.....

The figure represents a circuit.

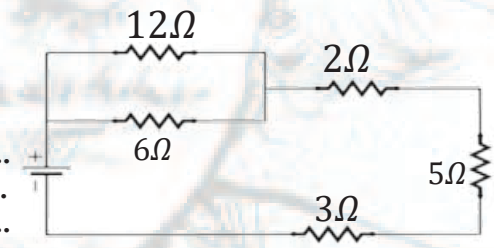

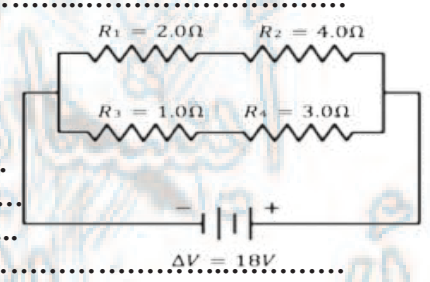
93
.....
.....
.....
.....

The figure represents a circuit.
3) Calculate the equivalent resistance in the circuit.
4) Calculate the total current in the circuit.



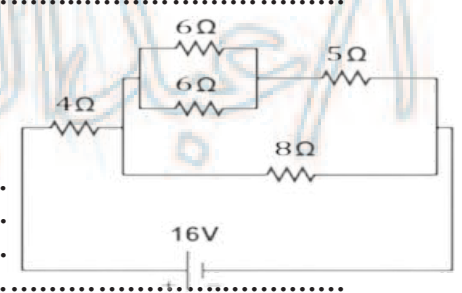
94
.....
.....
.....
.....

The figure represents a circuit.
1) Calculate the equivalent resistance in the circuit.
2) Calculate the total current in the circuit.




95
.....
.....
.....
.....

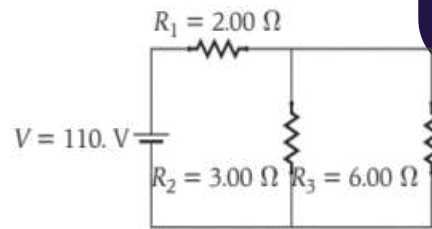
- 1) Find the potential drop across R_3 .
- 2) Find the current in R_1 .



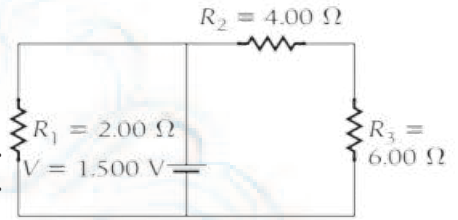
A battery with $V = 1.500 \text{ V}$ is connected to three resistors as shown in the figure.
Find the potential drop across each resistor.
Find the current in each resistor.




Idea

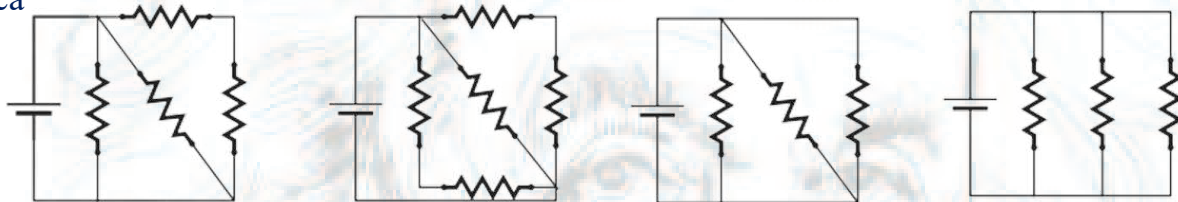

Idea

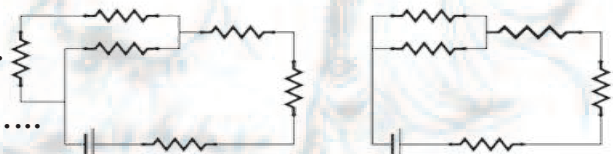

Idea

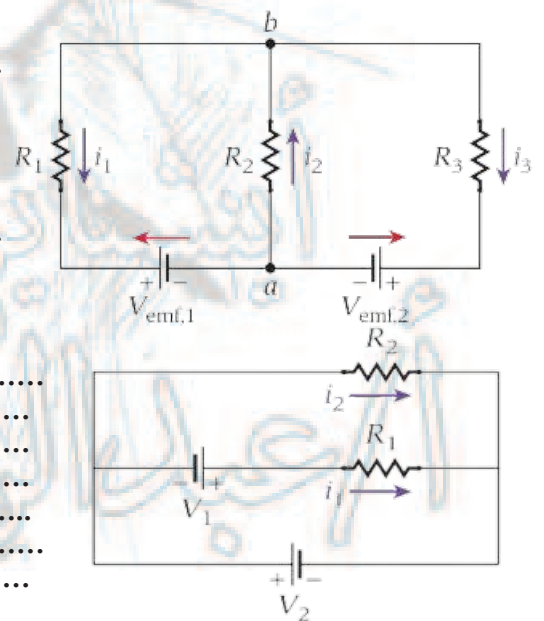

Idea