

This file was downloaded from the American Curriculum website



Gates Logic Basic about Worksheet الملف


[Almanahj Website](#) → [American curriculum](#) → [12th Grade](#) → [Physics](#) → [Term 1](#) → [The file](#)

More files for 12th Grade , Subject Physics , Term 1

Worksheet about Conversions for Physics and Chemistry	1
Worksheet about Physical Therapy	2
Worksheet about Ray diagram	3
Worksheet about physical world	4
Worksheet about Physical Therapy	5
Worksheet about Physical Therapy	6

Physical Computing

Basic logic gates

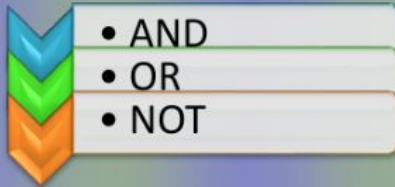

AND Gate



The following table shows whether the tank receives water or not from the main supply based on whether the A and B valves are closed or open.

A valve	B valve	Water supply to tank
Closed	Closed	does not receive water
Closed	Open	does not receive water
Open	Closed	does not receive water
Open	Open	receives water

A valve	B valve	Water supply to tank
0	0	
0	1	
1	0	
1	1	



The standard symbol for AND Gate

OR Gate



A valve	B valve	Water supply to tank
Closed	Closed	does not receive water
Closed	Open	receives water
Open	Closed	receives water
Open	Open	receives water

A valve	B valve	Water supply to tank
0	0	
0	1	
1	0	
1	1	





The standard symbol of the OR Gate

NOT Gate




Sun light	Electric lamp
available	OFF
unavailable	ON

Sun light	Electric lamp
1	
0	

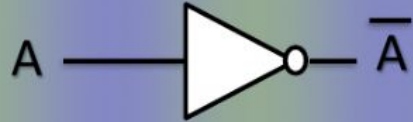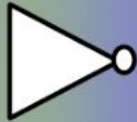


Standard Symbol of NOT gate


Connecting logic gates in circuits

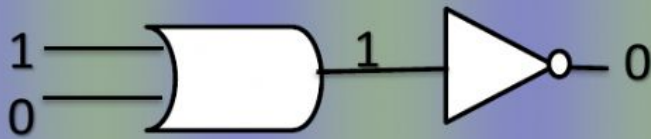


Obtaining the relevant output according to the input given In OR gate, the inputs are added to give the output ($1 + 0 = 1$)

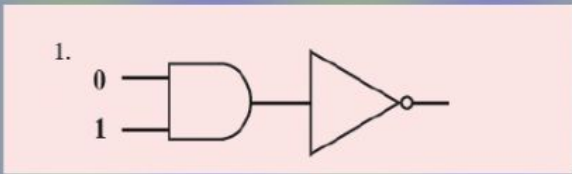Write down the output corresponding to the inputs given in the following circuits



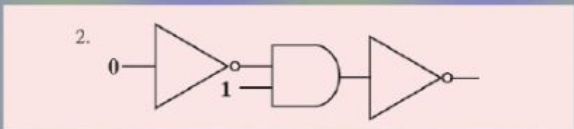

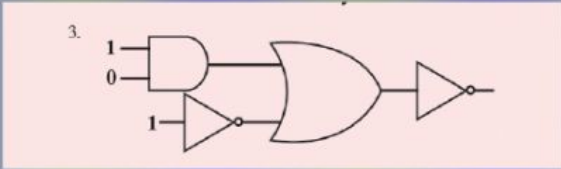

please watch this video